



Institute of Technology of Cambodia



Department of Electrical and Energy Engineering

Lab: MOTOR DRIVE

LECTURED BY:

MR. CHRIN PHOK (COURSE)

MR. SENG SOTHEA (TP)

STUDENT:

HENG RATANAKVISAL

ID: e20200074

CHHON CHANMAKARA

ID: e20200953

Group: I4-GEE-EA

ENGINEERING'S DEGREE

DEPARTMENT OF ELECTRICAL AND ENERGY ENGINEERING

INSTITUTE OF TECHNOLOGY OF CAMBODIA

PHNOM PENH

Academic Year:

2022-2023

TP4 : IGBT

Objective: To simulate to analyze Characteristics of IGBT

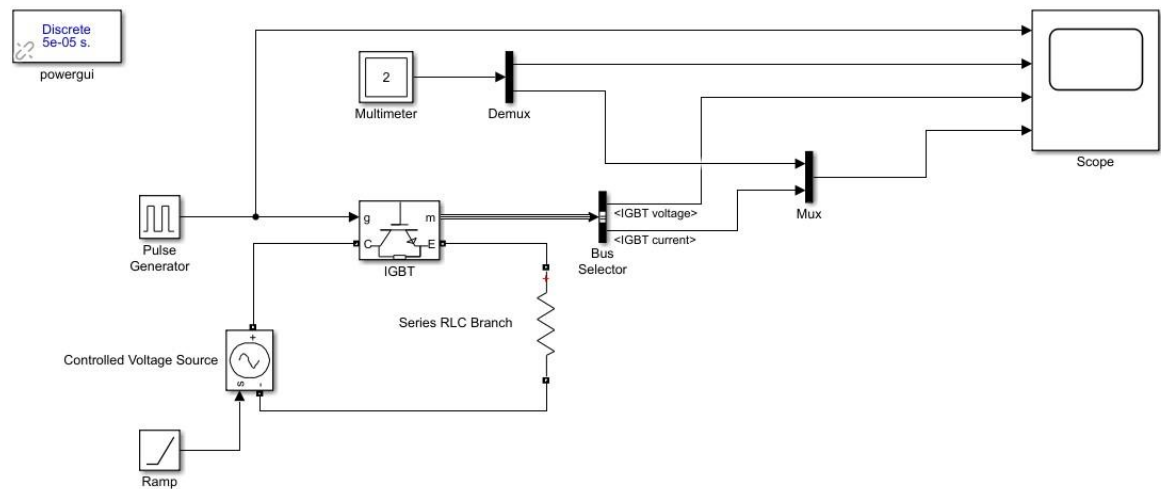


Figure 1: Block diagram of the circuit **Exercise**

Questions:

Describe meaning of the 4 outputs after the simulation for Forward Biased Mode and Backward Biased mode:

- Forward Biased Mode: Voltage across the load resistor and IGBT's current are on when the signal of the pulse generator is HIGH with the delay of pulse signal 1 period. For the IGBT's voltage start to turn on when the pulse signal is LOW and turn off to the default forward voltage when pulse generator is HIGH.

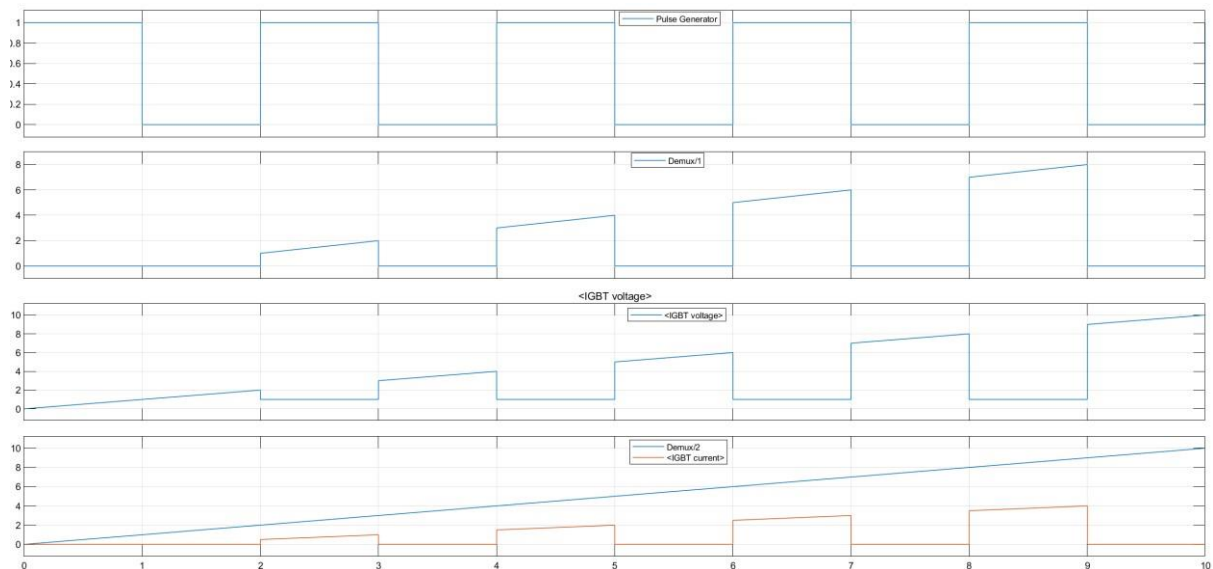


Figure 2: Response of the outputs in Forward Biased Mode

- Reverse Biased Mode: In this Mode, the voltage source flow in the opposite direction of the conventional current flow which makes all the voltages in the circuit leaning toward the negative values; while, there is no current flow in the circuit.

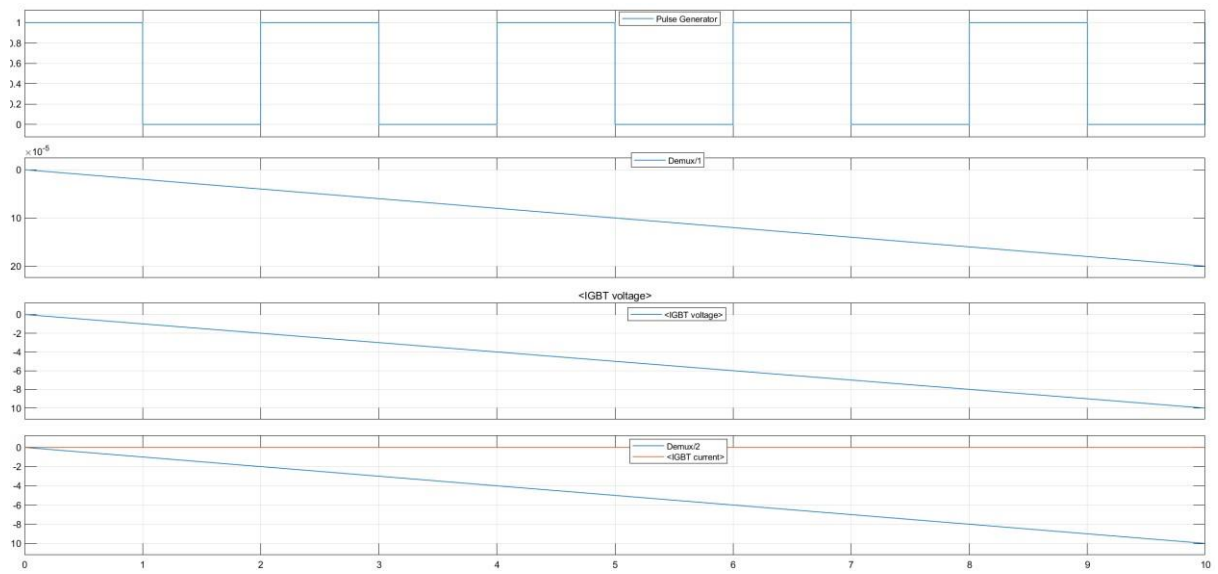


Figure 3: Response of the outputs in Backward Biased Mode