

### TP4 : IGBT

Objective: To simulate to analyze Characteristics of IGBT

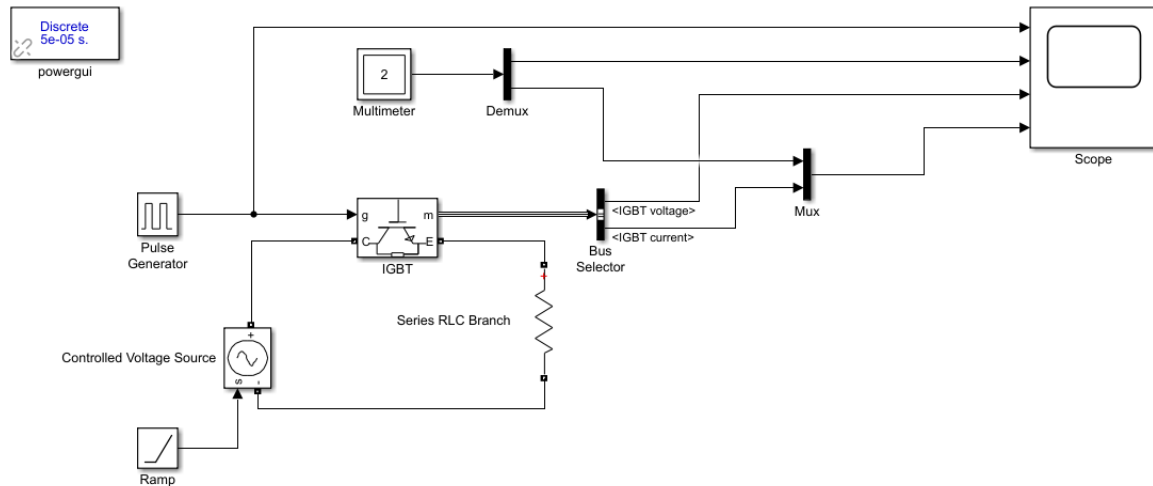


Figure 1: Block diagram of the circuit

#### Exercise Questions:

Descript meaning of the 4 outputs after the simulation for Forward Biased Mode and Backward Biased mode:

- Forward Biased Mode: Voltage across the load resistor and IGBT's current are on when the signal of the pulse generator is HIGH with the delay of pulse signal 1 period. For the IGBT's voltage start to turn on when the pulse signal is LOW and turn off to the default forward voltage when pulse generator is HIGH.

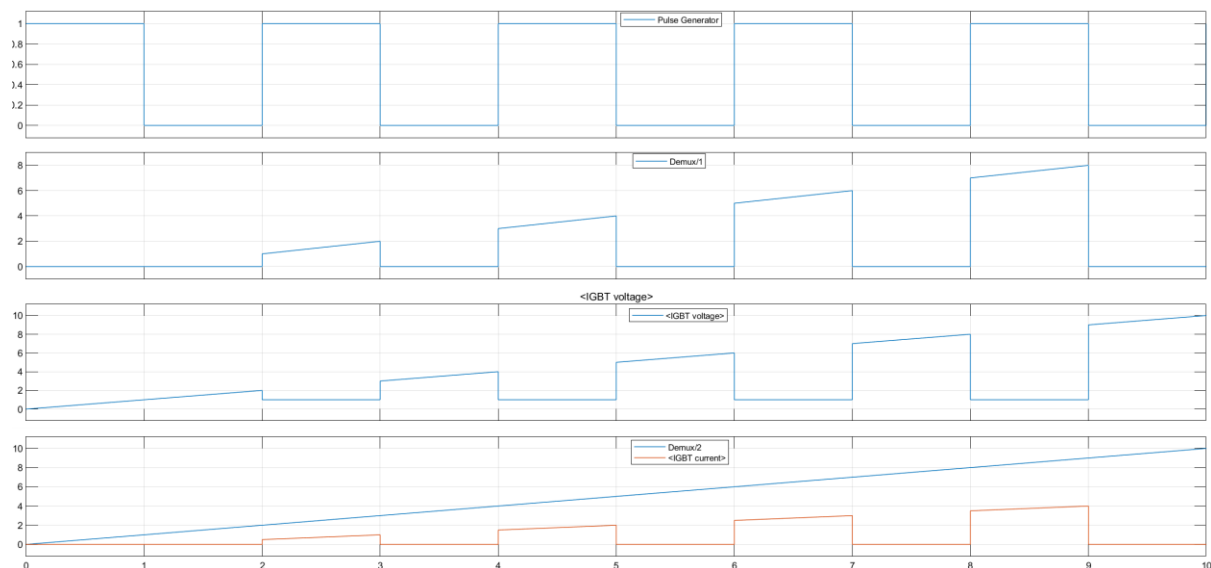


Figure 2: Response of the outputs in Forward Biased Mode

- **Reverse Biased Mode:** In this Mode, the voltage source flow in the opposite direction of the conventional current flow which makes all the voltages in the circuit leaning toward the negative values; while, there is no current flow in the circuit.

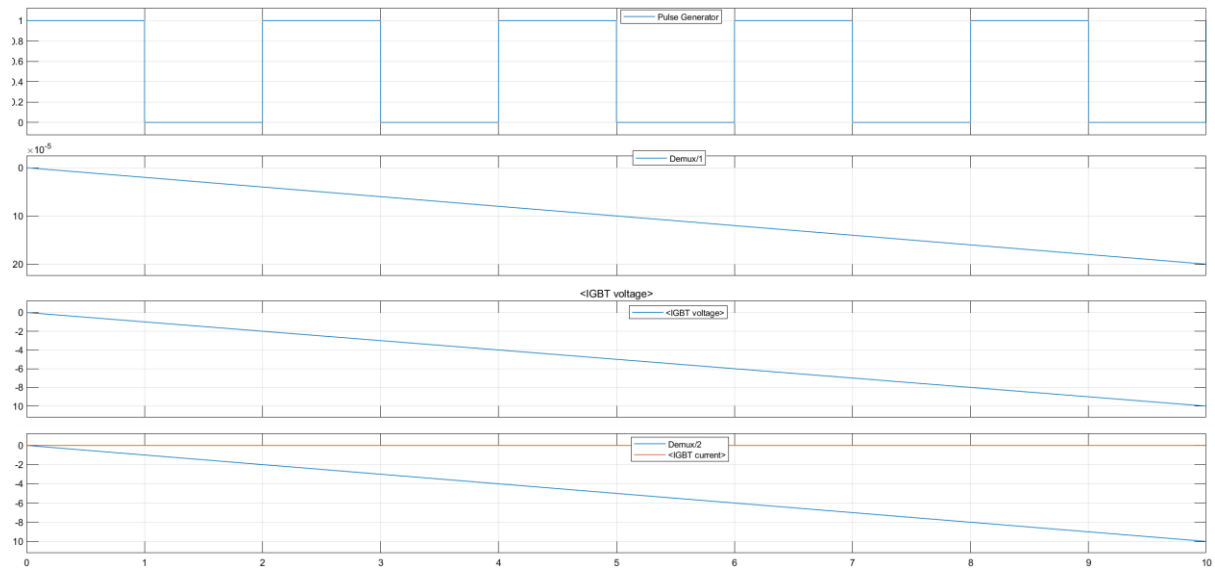


Figure 3: Response of the outputs in Backward Biased Mode